

Assignment - II

Page No. 01

Date :

Name : Mohsin Kumarkini

Class : BSc S.E. (FY) / A

Roll : A39


Subject : FDL

Assignment - II

Q1] What is gate? Explain basic gates.

- Gate or better known as logic gates is an electronic device, which has one or many inputs but only one output.
- Logic gates perform the operation on binary data, so gates are called basic building blocks of computer.

Types of Gates (Logic)

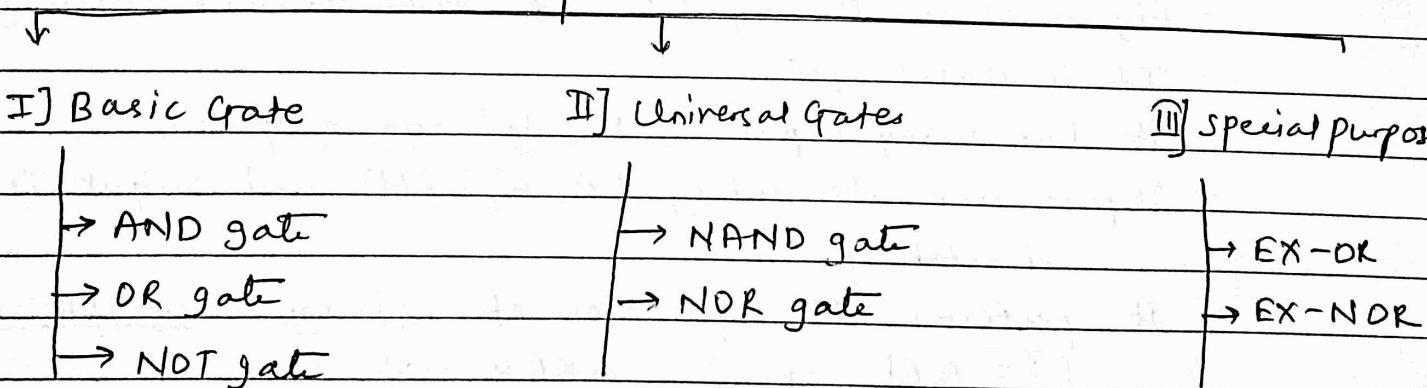

I] Basic Gates :-


- The gates which performs operation such as multiplication, addition and complementation is called basic gate.

There are 3 type of basic gates :-

- i) AND gate
- ii) OR gate
- iii) NOT gate

i) AND Gate :-

Symbol.

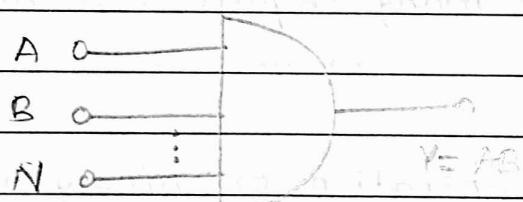

Truth Table

INPUT	OUTPUT
AB	Y
0 0	0
0 1	0
1 0	0
1 1	1

- figure shows the symbol and truth table of AND gate.
- It is Basic Gate.
- It has many inputs but only one output
- Inputs are denoted by (A, B, \dots, N) and output is denoted by (Y).
- It performs the operation of binary multiplication.


$$Y = A \cdot B \quad \text{or} \quad Y = A \cdot X \cdot B \cdot X \cdot \dots \cdot N$$

* Operation

- From the truth table, it is clear that:-

- When both inputs are '1', then output is always '1'.
- If anyone of the input is '0', then output is always '0'.

iii) OR Gate :-

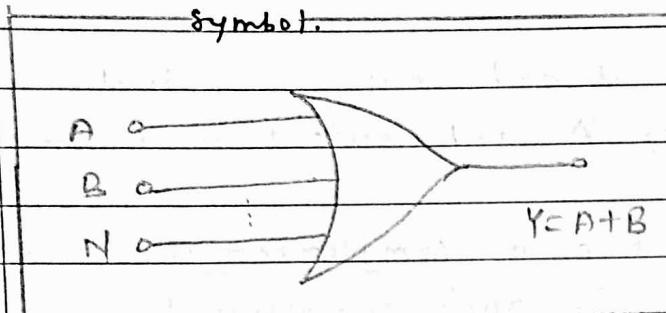

Truth-Table

INPUT A B	OUTPUT $Y = A + B$	Truth-Table			
		0 0	0 1	1 0	1 1
0 0	0				
0 1	1				
1 0	1				
1 1	1				

- figure shows the symbol and truth table of the OR gate.
- It is the Basic gate.
- It has many inputs but only one output.
- Input is denoted by (A, B, \dots, N) and output is denoted by (Y) .
- It performs the operation of binary addition.

$$Y = A + B + \dots + N$$


* Operation

- From the truth table it is clear that:-

- When both inputs are '0', then output is always '0'.
- When anyone of input is '1', output is always '1'.

iii) NOT Gate :-

Truth - Table

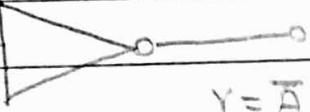symbol		INPUT	OUTPUT
	A	A	$Y = \bar{A}$
		0	1
		1	0

- figure shows the symbol and truth-table of NOT gate.
- It is the basic gate.
- It has only one input and only one output.
- Input is denoted by 'A' and output is denoted by 'Y'.
- It performs the operation of complementation. i.e. one's complement. In one's complement, '0' is replaced by '1' and '1' is replaced by '0'.
- NOT gate is also called as Inverter because output is completely reverse of the input.

* operation :-


- from the truth table, it is clear that:

- i) If input is '0', then output is always '1'.
- ii) If input is '1', then output is '0'.

Q2] Explain NAND and NOR gate.

Syn I] NAND gate:

-symbol

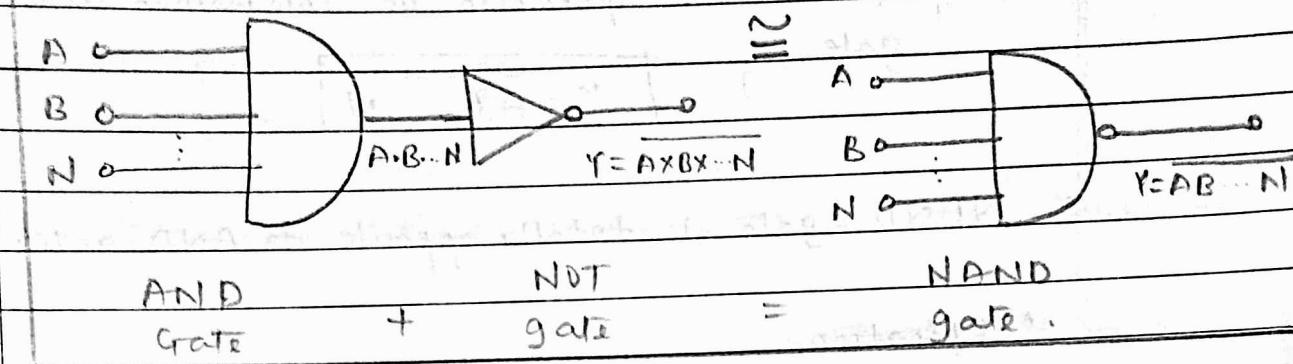

Truth-Table

	INPUT		OUTPUT
	A	B	$Y = \overline{AB}$
	0	0	1
	0	1	1
	1	0	1
	1	1	0

- figure shows the symbol and truth table of NAND gate.

- This is the universal gate. It is combination of two gates. i.e AND gate and NOT gate.


- It has many inputs but only one output.
- Inputs are denoted by (A, B, \dots, N) and outputs are denoted by (Y) .
- It performs the operation of complementation of AND gate.
i.e. $\therefore Y = \overline{A \cdot B \cdot \dots \cdot N}$
- NAND gate is totally opposite to AND gate.

* Operation:

- From truth table, it is clear that-
- i) When both the inputs are '1', then the output is always '0'.
- ii) If any one of the input is '0', then output is always '1'.

iii) NOR Gate:-

Symbol

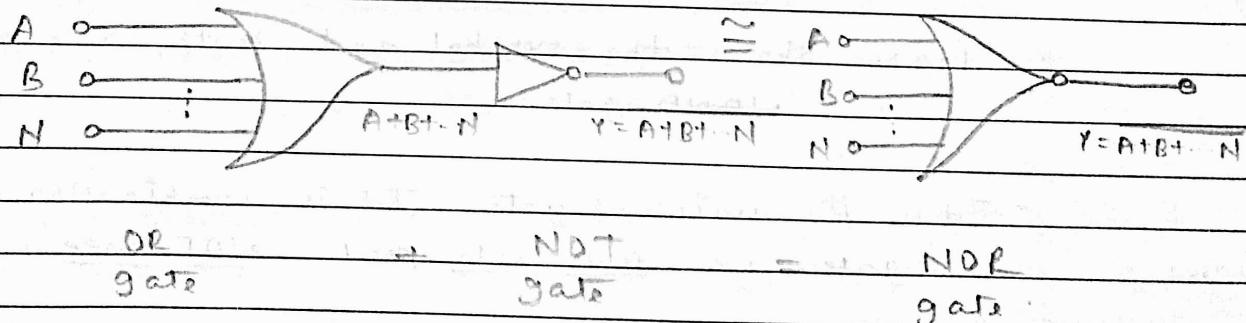

Truth Table

INPUT	OUTPUT
A+B	$Y = \overline{A+B}$
0 0	1
0 1	0
1 0	0
1 1	0

- figure shows that the symbol and truth table of NOR gate.
- It is universal gate. It is combination of two gates. i.e. OR gate and NOT gate
- It also has many inputs but only one output. Inputs are denoted by (A, B, \dots, N) and output is denoted by (Y)
- It performs the operation of complementation of OR gate.

$$\therefore Y = \overline{A+B+\dots+N}$$

- NOR gate is totally opposite to OR gate.

* Operation:


- from truth table, it is clear that:

- i) When both inputs are '0', then output is always '1'.
- ii) If anyone of the input is '1', then output is always '0'.

Q3] Explain EX-OR and EX-NOR gate:

→ i) EX-OR gate :-

symbol.

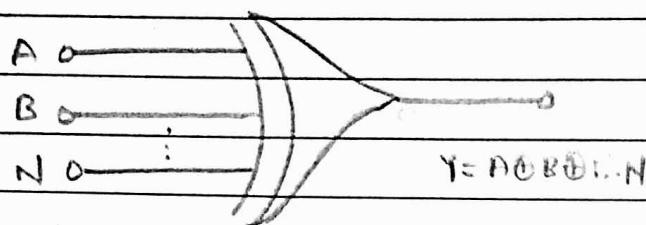

Truth - Table

INPUT	OUTPUT
AB	Y
0 0	0
0 1	1
1 0	1
1 1	0

- figure shows the symbol and truth-table of EX-OR gate.

- It is special purpose gate because they are used to compare the inputs.

- It has many inputs but only one output.

- Inputs are denoted by (A, B, \dots, N) and output is denoted by (Y)

- It performs the operation of EX-OR

$$\therefore Y = A \oplus B \oplus \dots \oplus N$$

- EX-OR operation is shown by + sign within a circle. \oplus

- Its operation is similar to OR-gate but the difference is in 4th row of the truth-table.

* Operation

i) When both inputs are same, then output is always '0'.


ii) If any both inputs are different, then output is always '1'.

* Operation

- +) When there are odd numbers of '1's, then output is always '1'.
- 2) When there are even number of '1's, then output is always '0'

iii) EX-NOR gate

Symbol

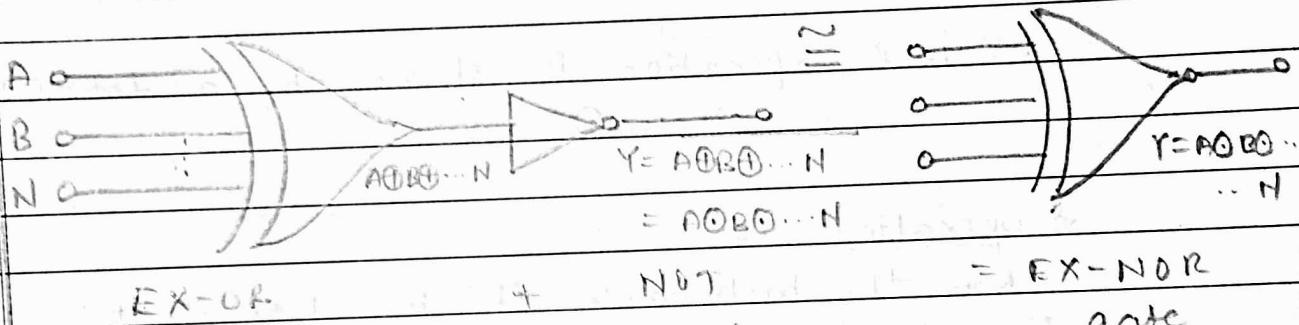

Truth-Table

INPUT	OUTPUT
A B	Y
0 0	1
0 1	0
1 0	0
1 1	1

- figure shows that the truth table and symbol of X-NOR or EX-NOR gate.

- It is special purpose gate.
- It has many inputs but only one output
- Inputs are denoted by (A, B, \dots, N) and output is denoted by (Y) .

- It performs the operation of EX-NOR

$$\therefore Y = A \odot B \odot \dots \odot N$$

- Its operation is similar to AND gate, but the difference is in the 1st row of truth table.

- EX-NOR operation is shown by a dot \odot within a circle \circ

* Operation

- From the truth table, it is clear that:

- i) When both inputs are same, output is always '1'
- ii) When both inputs are different, output is always '0'.


* operation

- 1) When there are even number of '1', then output is always '1'
- 2) When there are odd number of '1', then output is always '0'.

94]



Draw and explain full adder.

Logic diagram

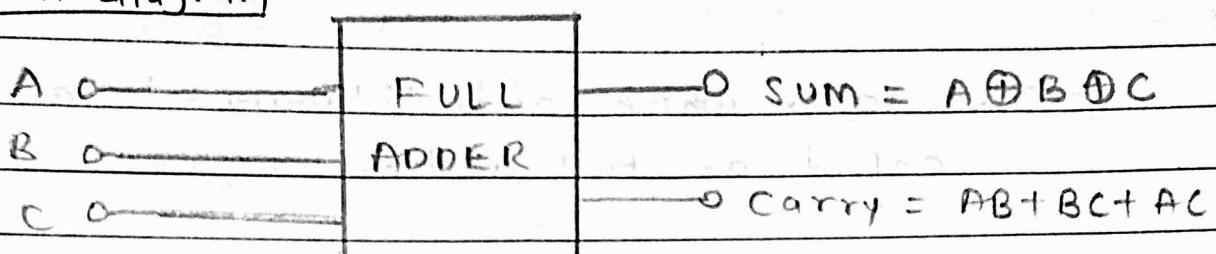

A B C

Circuit Diagram

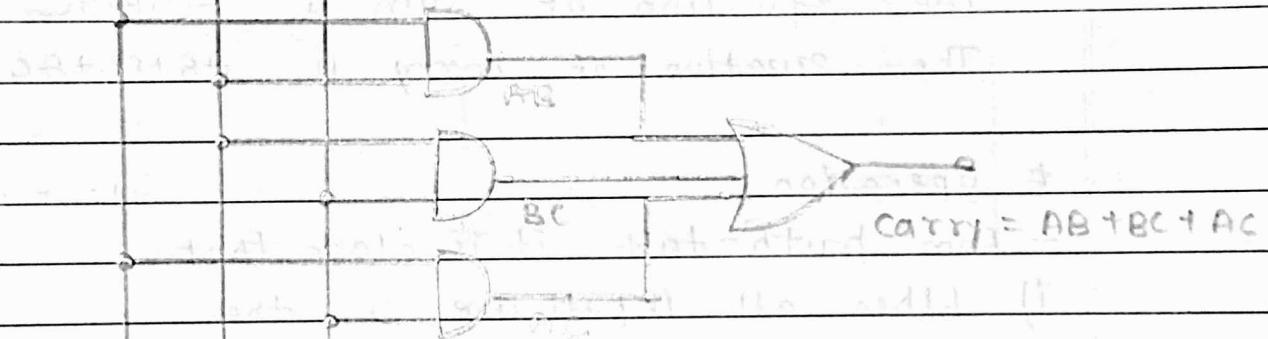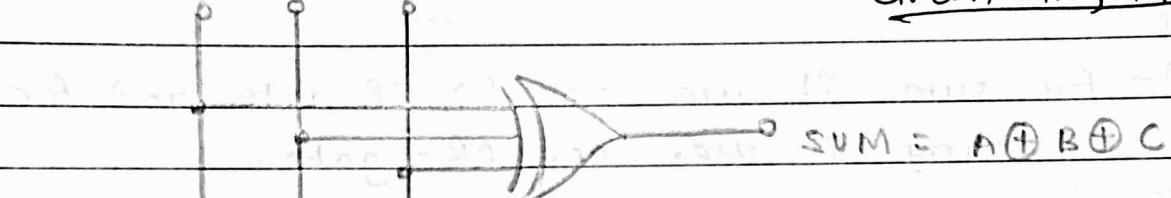

Truth-Table

INPUT			OUTPUT	
A	B	C	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- figure shows the logic diagram, circuit diagram and truth table of full adder.
- The adder which adds 3 binary bits at a time is called as full adder.
- It has 3 inputs (A, B, C) and two outputs (sum and carry).
- for sum, it uses one EX-OR gate and for carry, it uses one OR-gate.
- The equation of sum is $A \oplus B \oplus C$
The equation of carry is $AB + BC + AC$.

* Operation

- From truth-table it is clear that:

i) When all inputs are 0, then
 $sum = 0$, $carry = 0$.


ii) When any one of the input = 1,
 $sum = 1$, $carry = 0$.

iii) When any 2 inputs are 1,
 $sum = 0$, $carry = 1$,

iv) When all 3 inputs are 1,
 $sum = 1$, $carry = 1$.

Q5]

Draw and explain Half adder.

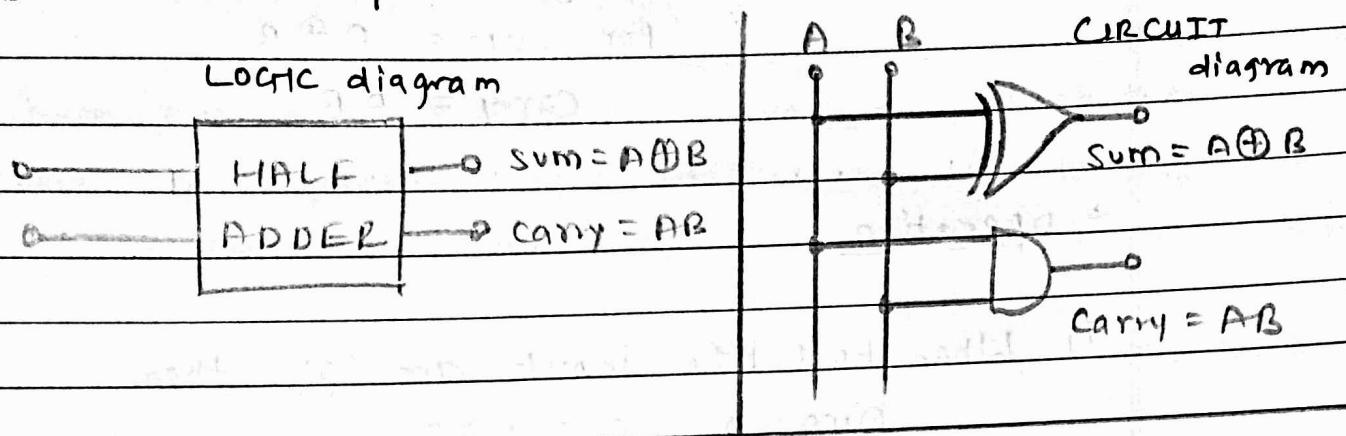

- figure shows the logic diagram, circuit diagram and truth table of half-adder.

- Half Adder :- The adder which adds two-binary bits at a time is called as half adder.

- It has two inputs (A and B) and two outputs (sum and carry).

- for sum, it uses EX-OR gate and for carry, it uses AND gate.

- The equation :

$$\text{for sum} = A \oplus B$$

$$\text{Carry} = A \cdot B$$

* operation :

i) When both the inputs are '0', then

$$\text{sum} = 0, \text{ carry} = 0.$$

ii) When any one of input is '1', then

$$\text{sum} = 1, \text{ carry} = 0.$$

iii) When both inputs are '1', then

$$\text{sum} = 0, \text{ carry} = 1.$$


Q61

State and prove De- Morgan's theorem.

→ There are two, De-Morgan's theorems, both are used to separate the variables from the bar (Complement).

I FIRST THEOREM :-
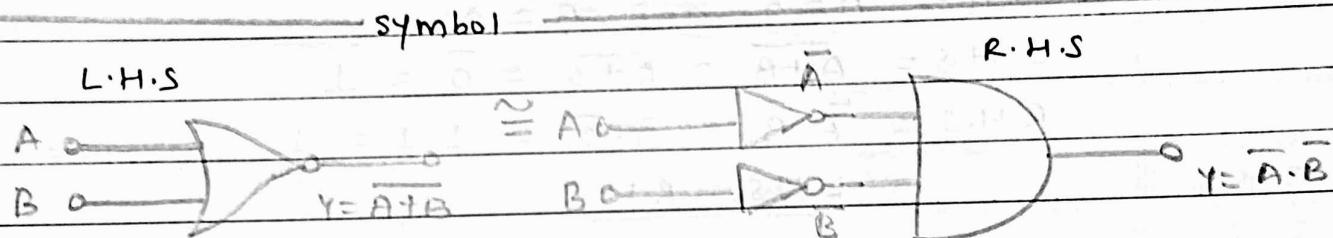
$$\overline{A+B} = \overline{A} \cdot \overline{B}$$



Truth-Table

INPUT	(L.H.S)	OUTPUT	(R.H.S)
A B	$A+B$	$\overline{A+B}$	$\overline{A} \cdot \overline{B}$
0 0	0	1	1
0 1	1	0	0
1 0	1	0	0
1 1	1	0	0

* Statement

- The complement of sum is equal to the product of their individual complement.
- From the truth table, it is clear that L.H.S = R.H.S
∴ Theorem is proved.

* Operation :

1) When $A=0$ and $B=0$

$$L.H.S = \overline{A+B} = \overline{0+0} = \overline{0} = 1$$

$$R.H.S = \overline{A} \cdot \overline{B} = \overline{0} \cdot \overline{0} = 1 \cdot 1 = 1$$

$$\therefore \underline{L.H.S = R.H.S}$$

2) When $A=0$ and $B=1$,

$$L.H.S = \overline{A+B} = \overline{0+1} = \overline{1} = 0$$

$$R.H.S = \overline{A} \cdot \overline{B} = \overline{0} \cdot \overline{1} = 1 \cdot 0 = 0$$

$$\therefore \underline{L.H.S = R.H.S}$$

3) When $A=1$, and $B=0$,

$$L.H.S = \overline{A+B} = \overline{1+0} = \overline{1} = 0$$

$$R.H.S = \overline{A} \cdot \overline{B} = \overline{1} \cdot \overline{0} = 0 \cdot 1 = 0$$

$$\therefore \underline{L.H.S = R.H.S}$$

4) When $A=1$ and $B=1$,

$$L.H.S = \overline{A+B} = \overline{1+1} = \overline{1} = 0$$

$$R.H.S = \overline{A} \cdot \overline{B} = \overline{1} \cdot \overline{1} = \overline{1} = 0$$


$$\therefore \underline{L.H.S = R.H.S}$$

Hence, theorem is proved.

II SECOND THEOREM

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

symbol

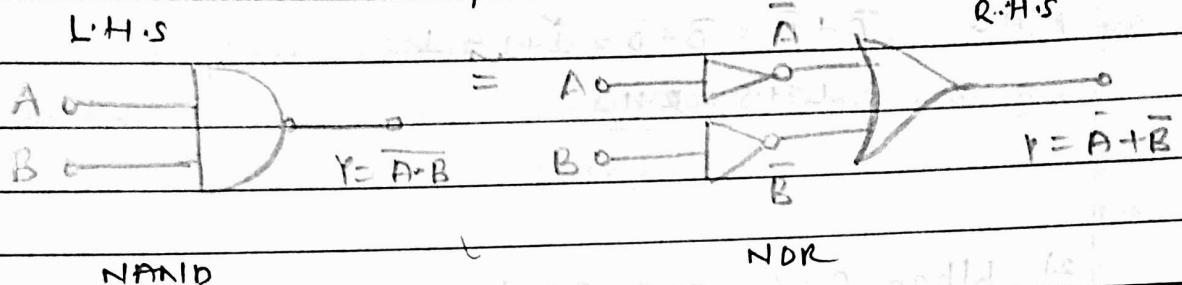

Truth-Table

INPUT		OUTPUT				
A	B	$A \cdot B$	$\overline{A \cdot B}$	\bar{A}	\bar{B}	$\bar{A} + \bar{B}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

Statement:

- The complement of product is equal to the sum of their individual complements.
 - from the truth table it is clear that - L.H.S = R.H.S
Hence theorem is proved.

operation:

1) When $A=0$, and $B=0$,

$$L.H.S = \overline{A \cdot B} = \overline{0 \cdot 0} = \overline{0} = 1$$

$$R.H.S = \overline{A} + \overline{B} = \overline{0} + \overline{0} = \overline{1+1} = 1$$

$$\therefore L.H.S = R.H.S$$

2) When $A=0$ and $B=1$,

$$L.H.S = \overline{A \cdot B} = \overline{0 \cdot 1} = \overline{0} = 1$$

$$R.H.S = \overline{A} + \overline{B} = \overline{0} + \overline{1} = 1 + 0 = 1$$

$$\therefore L.H.S = R.H.S$$

3) When $A=1$, and $B=0$,

$$L.H.S = \overline{A \cdot B} = \overline{1 \cdot 0} = \overline{0} = 1$$

$$R.H.S = \overline{A} + \overline{B} = \overline{1} + \overline{0} = 0 + 1 = 1$$

$$\therefore L.H.S = R.H.S$$

4) When $A=1$, and $B=1$,

$$L.H.S = \overline{A \cdot B} = \overline{1 \cdot 1} = \overline{1} = 0$$

$$R.H.S = \overline{A} + \overline{B} = \overline{1} + \overline{1} = 0 + 0 = 0$$

$$\therefore L.H.S = R.H.S$$


Theorem is proved.

Q7) Why NAND and NOR gate are called as Universal Gate?


→ NAND and NOR are called as universal gate because from NAND gate and NOR gate, we get the operation of any gate i.e. any basic gate (AND, OR and NOT).


I NAND as universal gate:

i) NOT gate using NAND gate

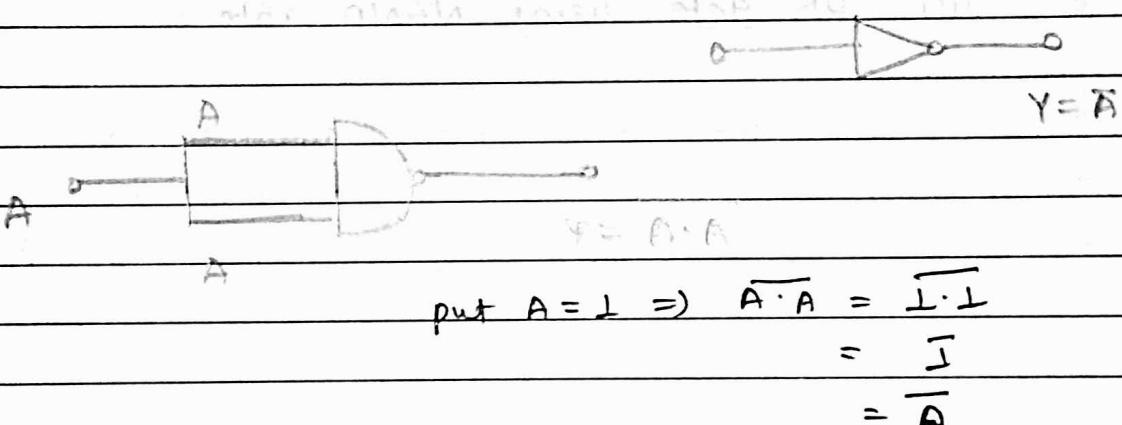

ii) AND gate using NAND gate:-

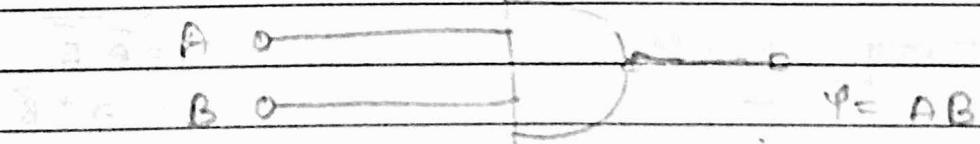

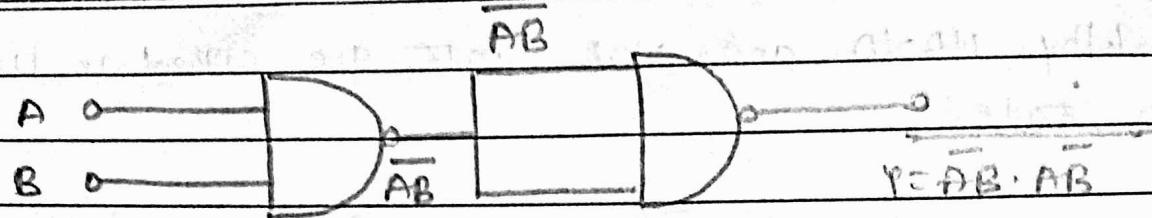

$$\text{put, } AB = 1 \Rightarrow Y = \overline{AB} \cdot \overline{AB}$$

$$= \overline{AB} + \overline{AB}$$


$$= AB + AB$$

$$= 1 + 1$$

$$= 1$$



$$= AB.$$

(iii) OR gate using NAND gate :

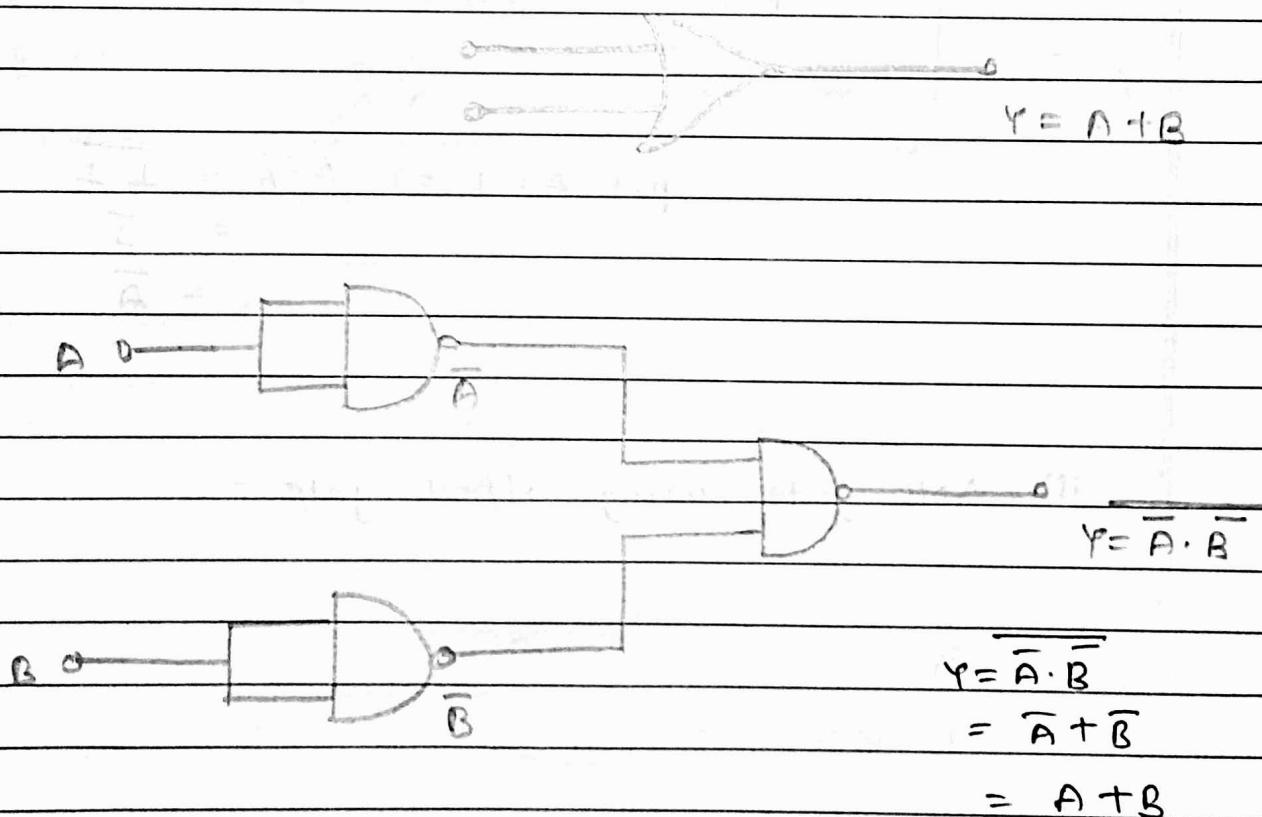

II NOR as a UNIVERSAL Gate:-




i) NOT gate using NOR gate:

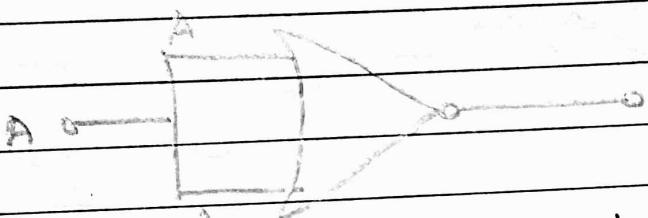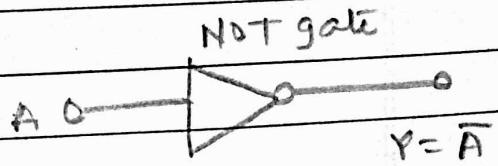

$$Y = \overline{A+A}$$

$$\begin{aligned} \text{put, } A=1 &\Rightarrow \overline{1+1} \\ &= \overline{1} \\ &= \overline{A} \end{aligned}$$

ii) OR gate using NOR gate.

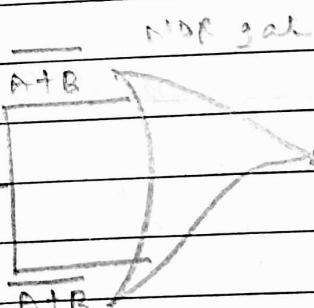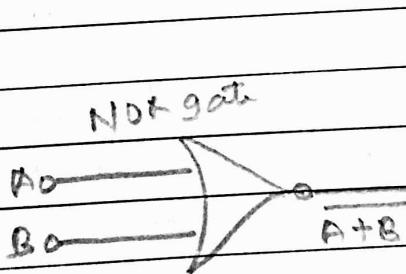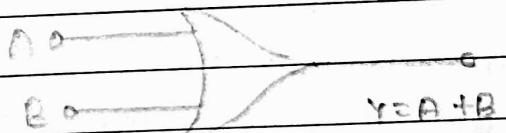

$$\begin{aligned} Y &= \overline{\overline{A+B} + \overline{A+B}} \\ &= \overline{\overline{A+B}} \cdot \overline{\overline{A+B}} \\ &= A+B \cdot A+B \end{aligned}$$

$$\begin{aligned} \text{put, } A+B=1 &\Rightarrow \overline{1} \cdot \overline{1} \\ &= \overline{1} \\ &= A+B \end{aligned}$$

iii) AND gate using NOR gate:

